



24.8200 Engineering Electromagnetics


ASSIGNMENT 7

Due Date: Tuesday December 5, 2006

Instructor: J. LoVetri

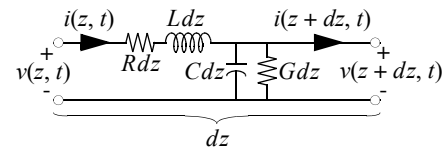- 1) (a) Show that the time-harmonic steady-state voltage and current on a transmission-line satisfy the one-dimensional Helmholtz equations

$$\begin{cases} \frac{d^2}{dz^2} V(z) - ZY V(z) = 0 \\ \frac{d^2}{dz^2} I(z) - ZY I(z) = 0 \end{cases}$$



where $Z = R + j\omega L$, $Y = G + j\omega C$, R , L , G , C , are the per-unit-length resistance [Ω/m], inductance [H/m], conductance [S/m], and capacitance [F/m] respectively, and ω is the angular frequency [rad/sec]. (Use the lumped-element model shown.)

- (b) Show that the solutions for waves, propagating in the positive z -direction, are given by

$$V^+ = V_0 e^{-\gamma z}, \quad I^+ = I_0 e^{-\gamma z}$$

where $\gamma = \sqrt{ZY}$ is the propagation constant.

- (c) Show that if $R \ll \omega L$ and $G \ll \omega C$

$$\alpha \approx \frac{R}{2\sqrt{L/C}} + \frac{G\sqrt{L/C}}{2} \quad \beta \approx \omega\sqrt{LC}$$

where $\gamma = \alpha + j\beta$, and determine the relationship between V_0 and I_0 .

- 2) Given the following inhomogeneous Sturm-Liouville system:

$$\text{(O.D.E.)} \quad \frac{d}{dx} \left[p(x) \frac{d\psi}{dx} \right] + [q(x) + \lambda s(x)] \psi = -f(x) \quad , \quad 0 \leq x \leq a$$

$$\text{(B.C.s)} \quad k_1 \psi(0) + k_2 \left. \frac{d\psi}{dx} \right|_{x=0} = k_3 \quad , \quad k_4 \psi(a) + k_5 \left. \frac{d\psi}{dx} \right|_{x=a} = k_6$$

where k_1, k_2, k_3, k_4, k_5 , and k_6 , are constants.

- a) Determine an appropriate ordinary differential equation and boundary conditions for the related Green's function problem.

- b) Express the solution to the above system, symbolically, in terms of the Green's function, $G(x; x')$, which is the solution of part (a).

- 3) Consider, first, the lossless transmission-line, ($R = G = 0$), with distributed time-harmonic current source $I_s(z)$ [A/m] (shunt). Derive the appropriate inhomogeneous Helmholtz equation for the voltage on this line and determine expressions for the voltage, $V(z)$, using the Green's function technique for the following four cases:
- (a) an infinite homogeneous transmission line;
 - (b) a semi-infinite ($z > 0$) transmission line short-circuited at $z = 0$;
 - (c) a semi-infinite ($z > 0$) transmission line open-circuited at $z = 0$; and
 - (d) a finite line ($0 < z < b$) terminated by impedances Z_a and Z_b .