

Modeling of Coupled Circuits

A-Gole
1995/Feb/7

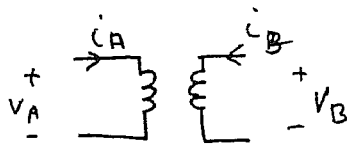



Fig 1: Transformer Windings

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} L_{AA} & L_{AB} \\ L_{BA} & L_{BB} \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_A \\ i_B \end{bmatrix} \quad - \text{ differential Equation for Coupled Circuit. } (1)$$

Let us evaluate L_{AA} , L_{BB} ... etc for a typical Transformer.

EX: Consider a 100 MVA transformer with a primary/secondary rated voltage of 100kV/50kV. Let the leakage inductance be 10% (distributed equally on both sides) and the magnetizing current is 1%.

Thus:

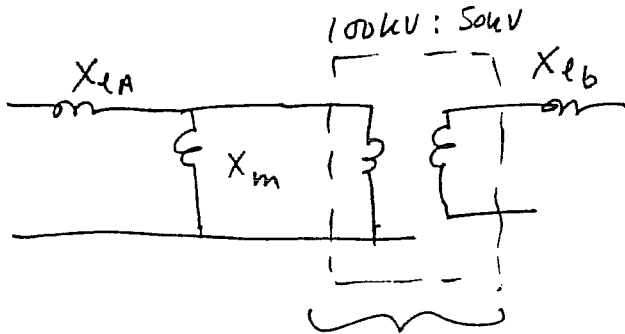

Ideal Transformer.

$$I_{base} = \frac{MVA_{base}}{KV_{base}} = 1 \text{ kA}$$

$$\therefore I_m = 1\% \times I_{base} = 0.01 \text{ kA}$$

$$\therefore X_m = \frac{KV_{base}}{I_m} = 10 \text{ k}\Omega$$

Fig 2: Transformer Equivalent Circuit

$$Z_{base} = \frac{KV_{base}^2}{MVA_{base}} = 100 \Omega$$


$$\therefore X_{lA} = \frac{10\%}{2} \times 100 \Omega = 5 \Omega$$

$$X_{lB} = \frac{10\%}{2} \times 25 \Omega = 1.25 \Omega$$

$$\therefore L_{lA} = 13.26 \text{ mH}, L_{lB} = 3.32 \text{ mH}, L_m = 26.526 \text{ mH}$$

assuming $\omega_0 = 377 \text{ rad/s}$

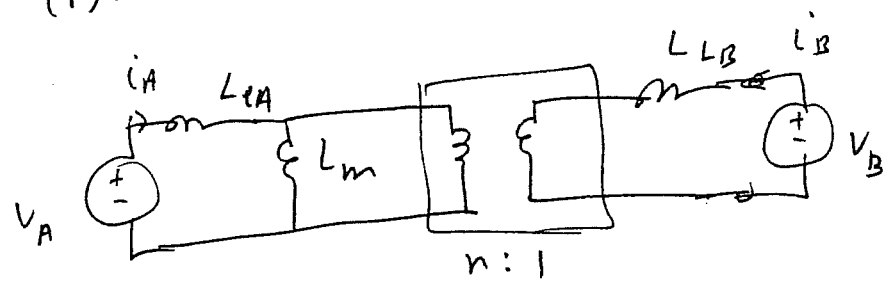Let us now try to obtain the circuit equations in the form (1).



We see that

$$V_A = L_{EA} \frac{di_A}{dt} + L_m \frac{d}{dt} \left(i_A + \frac{i_B}{n} \right)$$

$$V_B = \frac{1}{n} \left[L_m \frac{d}{dt} \left(i_A + \frac{i_B}{n} \right) \right] + L_{EB} \cdot \frac{d}{dt} i_B$$

Thus:

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} L_{EA} + L_m & \frac{L_m}{n} \\ \frac{L_m}{n} & \frac{L_m}{n^2} + L_{EB} \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_A \\ i_B \end{bmatrix}$$

Thus:

$$L_{EA} + L_m = L_{AA}, \quad \frac{L_m}{n} = L_{AB} = L_{BA}$$

$$\frac{L_m}{n^2} + L_{EB} = L_{BB}.$$

Obtaining an admittance matrix formulation

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = \mathcal{L} \frac{d}{dt} \begin{bmatrix} i_A \\ i_B \end{bmatrix} \quad - (1)$$

Thus:

$$\begin{bmatrix} i_A \\ i_B \end{bmatrix} = \mathcal{L}^{-1} \int_{t-\Delta t}^t \begin{bmatrix} V_A \\ V_B \end{bmatrix} dt + \begin{bmatrix} i_A(t-\Delta t) \\ i_B(t-\Delta t) \end{bmatrix}$$

\Downarrow
 $\underline{i(t)}$

By Trapezoidal Rule

(3)

$$\begin{aligned}\underline{i}(t) &= \mathcal{L}^{-1} \frac{\underline{v}(t) + \underline{v}(t-\Delta t)}{2} \cdot \Delta t + \underline{i}(t-\Delta t) \\ &= \mathcal{L}^{-1} \frac{\Delta t}{2} \underline{v}(t) + \left[\underline{i}(t-\Delta t) + \frac{\mathcal{L}^{-1} \underline{v}(t-\Delta t) \Delta t}{2} \right] \\ &= \underbrace{\underline{S}}_{\substack{\text{Admittance} \\ \text{matrix.}}} \underline{v}(t) + \underbrace{\underline{I}_h(t-\Delta t)}_{\text{History Term}} \quad - (2)\end{aligned}$$

Now each element of $\underline{i}(t)$ is the current in a branch connected (say) between nodes k and m . Similarly each element of \underline{v} is $v_k - v_m$ where v_k and v_m are node voltages. We now write the KCL equations at node k or m by including the term $+i_{km}$ at node k or $-i_{km}$ at node m . Note that $i_{km} = s_1' v_1 + s_2' v_2 + \dots + s_n' v_n + i_{hkm}(t-\Delta t)$ from eqn. 2. Thus at node k ,

$$\begin{aligned}0 &= -g_{1k} v_1 - g_{2k} v_2 \dots + (g_{k1} + g_{k2} + \dots + g_{kn}) v_k - \dots - g_{nk} v_n \\ &\quad - J_k + I_{hk}(t-\Delta t) \\ &\quad + (+s_1' v_1 + s_2' v_2 \dots + s_n' v_n) + i_{hkm}(t-\Delta t) \quad - (3)\end{aligned}$$

where as before, g_{1k}, \dots etc. are the admittances to other branches, J_k is the current injection from external sources and $I_{hk}(t-\Delta t)$ is the history term injection.

The coefficients s_1' etc. are from the appropriate row of (2) corresponding to transformer branch currents ... into transformer branches connected at node k .

Thus:

$$(-g_{1k} - s_1') V_1 + (-g_{2k} - s_2') V_2 \dots + (g_{k1} + \dots + g_{kn} - s_k') V_k + \left(\sum_n g_{nk} \right) V_n = J_k - I_{nk}(t-0^+) + i_{nk}(t-0^+).$$

Similarly all other KCL equations are developed, and we obtain for the network, the familiar form:

$$[Y] \underline{V}(t) = \underline{J}(t) - \underline{I}_h(t-0^+) \quad (5)$$

which is then solved in the usual manner.

Example:

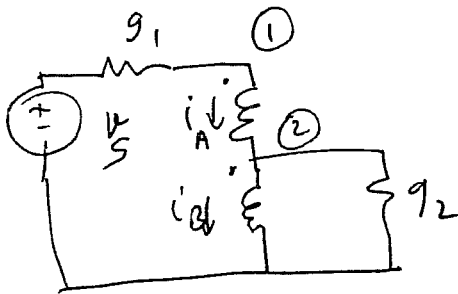


Fig 4: Coupled Circuit

$$\begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{bmatrix} L_{AA} & L_{AB} \\ L_{BA} & L_{BB} \end{bmatrix}^{-1} \frac{\Delta t}{Z} \begin{pmatrix} V_A \\ V_B \end{pmatrix} + \begin{bmatrix} I_{LA}(t-0^+) \\ I_{LB}(t-0^+) \end{bmatrix} \quad (6)$$


In the form of Eqn. 2.

We assign node numbers as shown (1 & 2) in Fig 4. The history terms in the above equation have the form:

$$\text{where } I_{LA}(t-\Delta t) = I_A(t-\Delta t) + S_{AA} [V_1(t-\Delta t) - V_2(t-\Delta t)] + S_{AB} (V_2(t-\Delta t)) \quad (6)$$

$$I_{LB}(t-\Delta t) = I_B(t-\Delta t) + S_{BA} [V_1(t-\Delta t) - V_2(t-\Delta t)] + S_{BB} V_2(t-\Delta t). \quad (7)$$

Let us write KCL at node ① and ②

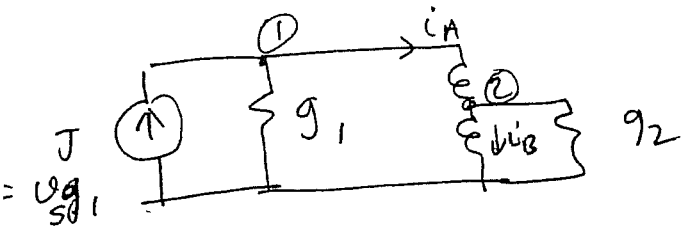

$$\left. \begin{aligned} -J + g_1 V_1 + i_A &= 0 \\ -i_A + i_B + g_2 V_2 &= 0 \end{aligned} \right\} \quad (8)$$

expanding for $i_A = S_{AA} V_A + S_{AB} V_B + I_{LA}(t-\Delta t)$

and for $i_B = S_{BA} V_A + S_{BB} V_B + I_{LB}(t-\Delta t)$

and realizing that $V_A = V_1 - V_2$, $V_B = V_2$, we

get:

$$-J + g_1 V_1 + S_{AA} (V_1 - V_2) + S_{AB} \cdot V_2 + I_{LA}(t-\Delta t) = 0$$

$$-S_{AA} (V_1 - V_2) - S_{AB} V_2 - I_{LA}(t-\Delta t) + S_{BA} (V_1 - V_2) + S_{BB} V_2 + I_{LB}(t-\Delta t) = 0$$


$$\text{or } \begin{bmatrix} g_1 + S_{AA} & -S_{AA} - S_{AB} \\ -S_{AA} + S_{BA} & S_{AA} - S_{AB} - S_{BA} + S_{BB} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} J - I_{LA}(t-\Delta t) \\ + I_{LA}(t-\Delta t) - I_{LB}(t-\Delta t) \end{bmatrix}$$

-(9)

$$\text{or } [Y]V(t) = \underline{I}(t-\Delta t) \quad (6)$$

and $V(t)$ can be evaluated in the standard manner. The history terms for the next time-step are evaluated from (7) and the currents in the windings from (6).

State Variable Formulation

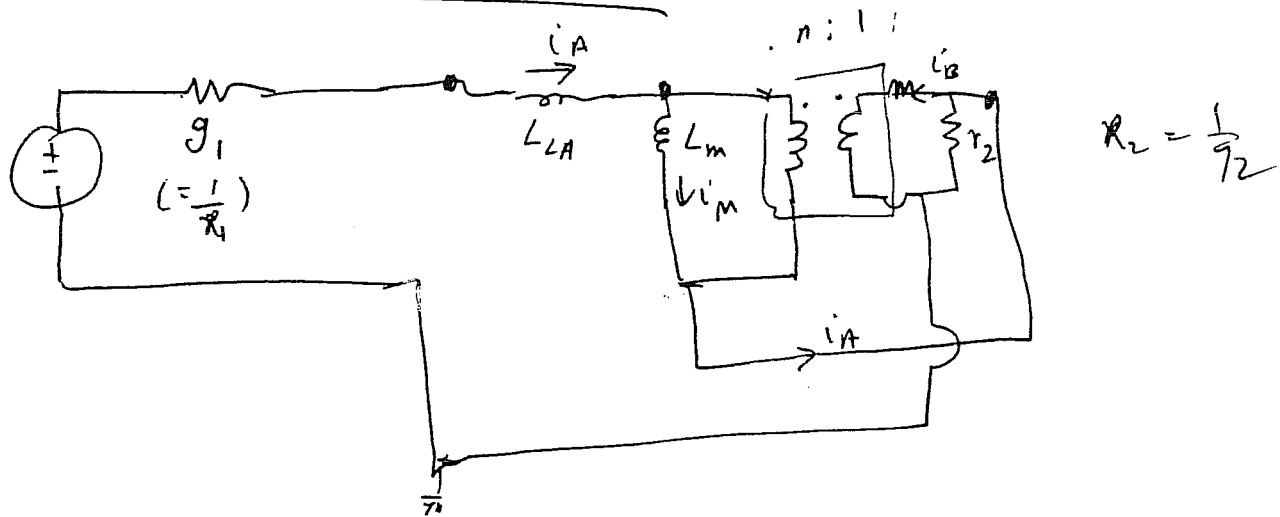

Choose i_A, i_B as state variables. Only 2 can be chosen because the three are not linearly independent. Then $i_m = i_A + \frac{i_B}{n}$

VL equations give:

$$V_s - R_1 i_A - L_m \frac{di_m}{dt} - L_{LA} \frac{di_A}{dt} + R_2 (i_A - i_B) = 0$$

$$\text{so } (i_A - i_B) R_2 - L_B \frac{di_B}{dt} = L_m \frac{di_m}{dt} \cdot \frac{1}{n}$$

Thus:

$$V_S - R_1 i_A - L_m \frac{d}{dt} \left(i_A + \frac{i_B}{n} \right) + R_2 (i_A - i_B) = 0$$

$$- L_{LA} \frac{di_A}{dt}$$

$$(i_A - i_B) R_2 - \frac{L_{LB}}{n} \frac{di_B}{dt} = \frac{1}{n} \cdot L_m \left[i_A + \frac{i_B}{n} \right]$$

Thus:

$$\begin{bmatrix} -L_m - L_{LA} & -\frac{L_m}{n} \\ -\frac{L_m}{n} & -L_{LB} - \frac{L_m}{n^2} \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} -V_S \\ 0 \end{bmatrix} + \begin{bmatrix} R_1 + R_2 & -R_2 \\ R_2 & R_2 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix}$$

$$\text{or } \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{bmatrix} \mathcal{L} \end{bmatrix}^{-1} \begin{bmatrix} \mathcal{R} \end{bmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} \neq \begin{bmatrix} -V_S \\ 0 \end{bmatrix}$$

$$\underline{\dot{X}} = \underline{A} \underline{X} + \underline{B} \underline{U}$$

