

## Transmission Line Equations

the telegrapher's equations are given as :

$$\left\{ \begin{array}{l} \text{PDEs} \\ \partial_x v(x,t) + L \partial_t i(x,t) + R i(x,t) = V_f(x,t) \\ \partial_x i(x,t) + C \partial_t v(x,t) + G v(x,t) = I_f(x,t) \end{array} \right. \quad \begin{array}{l} 0 < x < l \\ 0 < t \end{array}$$

$v(x,t)$  - voltage on the line

$i(x,t)$  - current on the line

$L$  - p.u.l. inductance

$C$  - p.u.l. capacitance


$R$  - p.u.l. series resistance

$G$  - p.u.l. shunt capacitance

$V_f(x,t)$  - distributed voltage source

$I_f(x,t)$  - distributed current source.

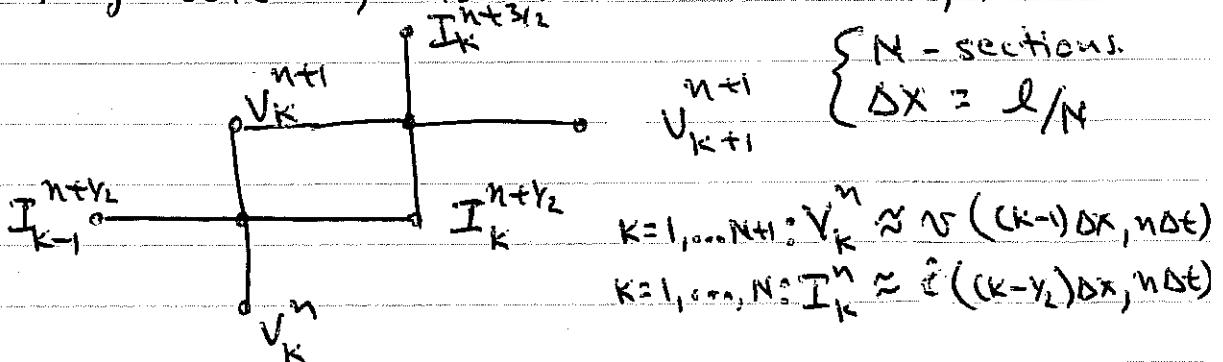the computational molecule for the inter-laced leap-frog scheme, also known as FDTD, is



Note: we're only using  $\gamma_2$ -index notation for time. -1-

Using 2<sup>nd</sup>-Order centred finite differences  
for discretizing the PDE's:

$$\frac{V_{k+1}^{n+1} - V_k^{n+1}}{\Delta x} + L \frac{I_k^{n+3/2} - I_k^{n+1/2}}{\Delta t} + R \frac{I_k^{n+3/2} + I_k^{n+1/2}}{2} = \frac{V_{Fk}^{n+3/2} + V_{Fk}^{n+1/2}}{2}$$

$$\frac{I_{k+1}^{n+1/2} - I_{k-1}^{n+1/2}}{\Delta x} + C \frac{V_k^{n+1} - V_k^n}{\Delta t} + G \frac{V_k^{n+1} + V_k^n}{2} = \frac{I_{Fk}^{n+1} + I_{Fk}^n}{2}$$

Solving for  $I_k^{n+3/2}$  and  $V_k^{n+1}$ :

$$\left( L \frac{\Delta x}{\Delta t} + \frac{R}{2} \Delta x \right) I_k^{n+3/2} = \left( L \frac{\Delta x}{\Delta t} - \frac{R}{2} \Delta x \right) I_k^{n+1/2} - (V_{k+1}^{n+1} - V_k^{n+1}) + \frac{\Delta x}{2} (V_{Fk}^{n+3/2} + V_{Fk}^{n+1/2})$$


$$\left( C \frac{\Delta x}{\Delta t} + \frac{G}{2} \Delta x \right) V_k^{n+1} = \left( C \frac{\Delta x}{\Delta t} - \frac{G}{2} \Delta x \right) V_k^n - (I_k^{n+1/2} - I_{k-1}^{n+1/2}) + \frac{\Delta x}{2} (I_{Fk}^{n+1} + I_{Fk}^n)$$

These are the general update equations.

Now we need to look at incorporating the boundary conditions:

$$\begin{cases} v(0,t) = V_s - R_s i(0,t) \\ v(l,t) = V_f + R_f i(l,t) \end{cases}$$

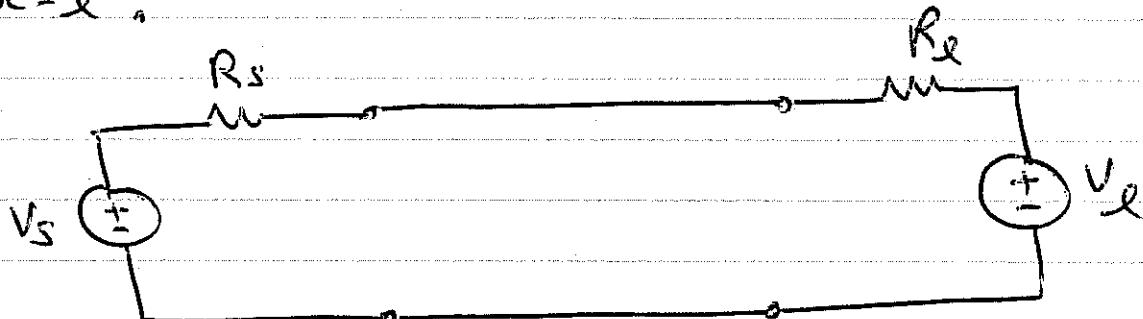These boundary conditions represent Thévenin Equivalent sources at  $x=0$  and  $x=l$ .



These can be converted to Norton equivalents in order to better incorporate them into the Finite-difference scheme?



$I_0 = I_{N+} = 0$  because the line ends at  $x=0$ ,  $x=l$ , the first current is  $I_1$ , and the last current is  $I_N$

Thus, at the first cell we have:

$$\left\{ \begin{array}{l} I_0 = 0 \\ G_T = G_S / \Delta x = \frac{1}{R_S \Delta x} \text{ equivalent parallel conductance} \\ I_{FO}^T = \frac{V_S}{R_S \Delta x} \text{ equivalent parallel current source} \end{array} \right.$$

and at the final cell?

$$\left\{ \begin{array}{l} I_N = 0 \\ G_N^T = \frac{G_L}{\Delta x} = \frac{1}{R_L \Delta x} \end{array} \right. \begin{array}{l} \text{equivalent p.u.l} \\ \text{conductance} \end{array}$$
$$I_{FN}^T = \frac{V_L}{R_L \Delta x} \quad \begin{array}{l} \text{equivalent p.u.l} \\ \text{current source.} \end{array}$$

$G_C^T$  and  $G_N^T$  add to whatever conductance is already at these cells.

$I_{FO}^T$  and  $I_{FN}^T$  also add to whatever current sources are already at these cells.

So the same up-date equation can be used after these replacements have been made.